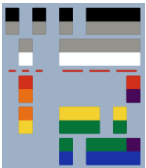





# INTRODUCTION TO FEEDBACK SYSTEM



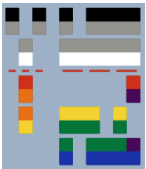
# Topic Outcomes

- Discuss the concept of negative feedback
- Differentiate feedback connection types
- Compute parameters with feedback connections





# Feedback

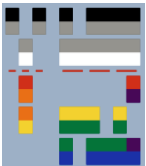

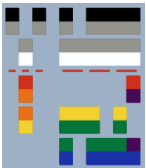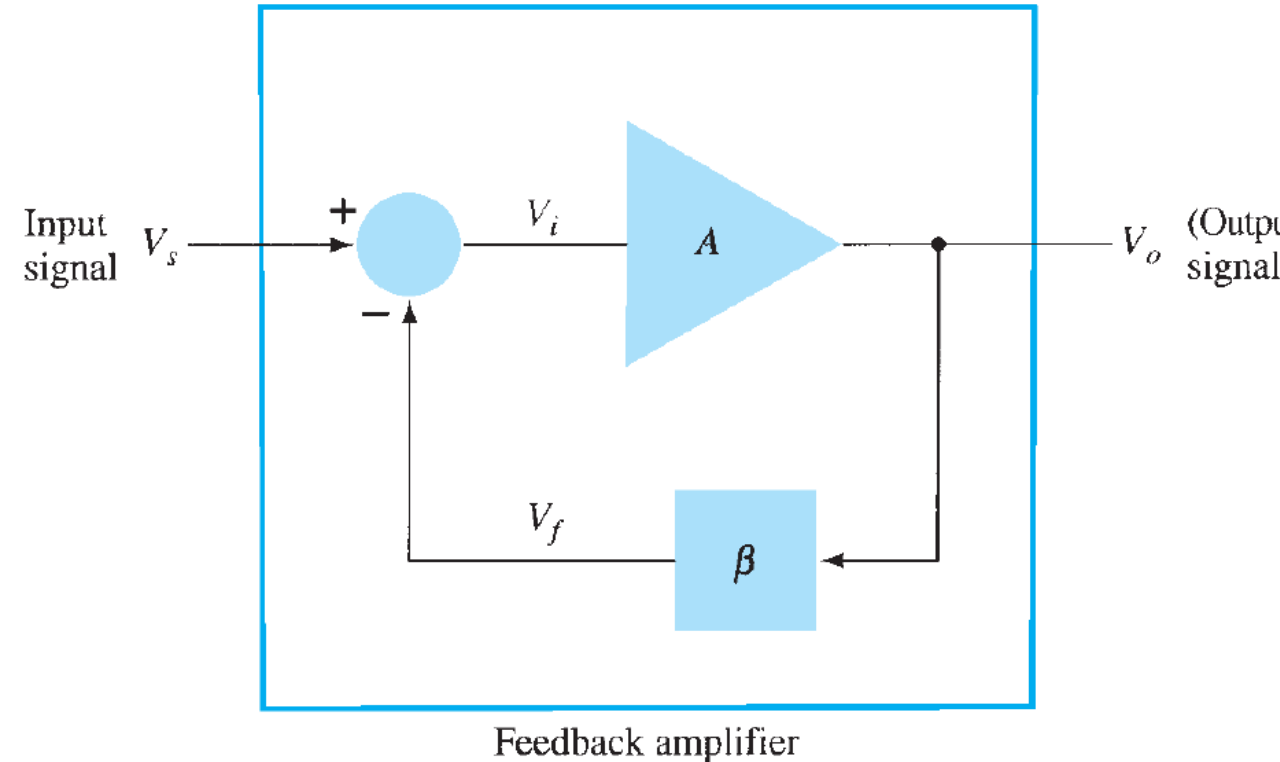
# Feedback

- A circuit may have positive or negative feedback depending on the polarity of the signal being fed back to the system.
- Positive feedback drives a circuit into oscillation, while negative feedback decreases the voltage gain of the system but improves a number of circuit features.
- A simple block diagram of a feedback amplifier system is shown in the figure. Input Signal  $V_s$  is applied to mixer circuit combined with the feedback signal,  $V_f$ .
- The difference of  $V_s$  and  $V_f$  is the input voltage of the amplifier  $A$ . Then the output voltage  $V_{out}$  is connected to the feedback circuit that causes reduction to the output signal as feedback signal to the input mixer network.



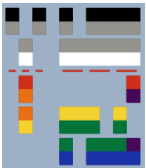
# Feedback

- In negative feedback, the polarity of the input signal is opposite to the feedback signal.
- Negative feedback reduces overall voltage gain but improves the following areas:
  1. Higher input impedance
  2. Better stabilized voltage gain
  3. Improved frequency response
  4. Lower output impedance
  5. Noise Reduction
  6. More linear operation



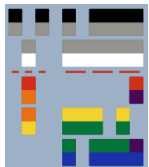
# Feedback


- There are four basic ways to implement feedback signal to other system. Both voltage and current may be fed back to the input to a system either in series or parallel.
  - Voltage refers to connecting the output voltage as input to the feedback network.
  - Current refers to tapping off some output current through the feedback network.
  - Series refers to connecting the feedback signal in series with the input signal voltage.
  - Shunt refers to connecting the feedback signal in shunt (parallel) with an input current source.




# Feedback Connection Types

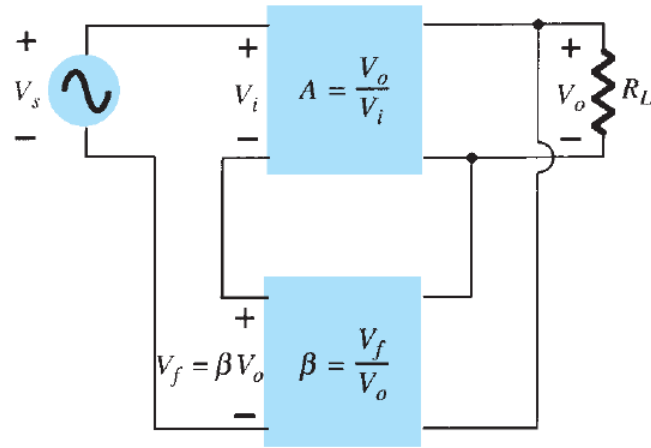


**Voltage-series feedback**

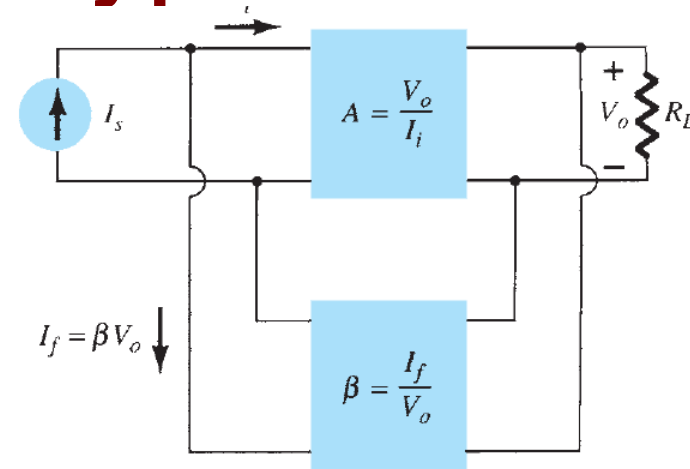


**Voltage-shunt feedback**

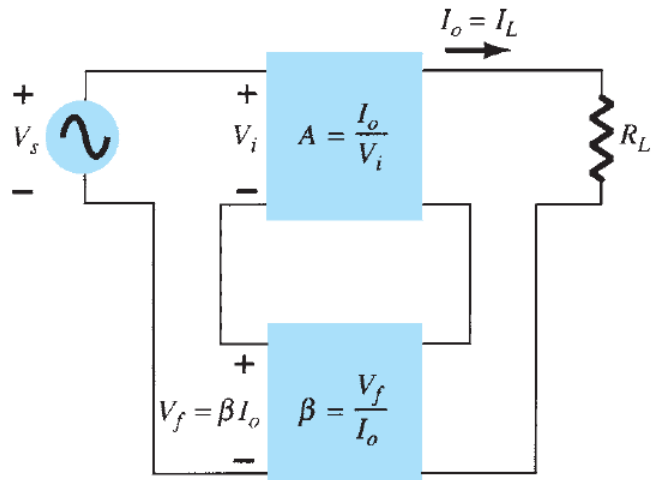

**Current-series feedback**

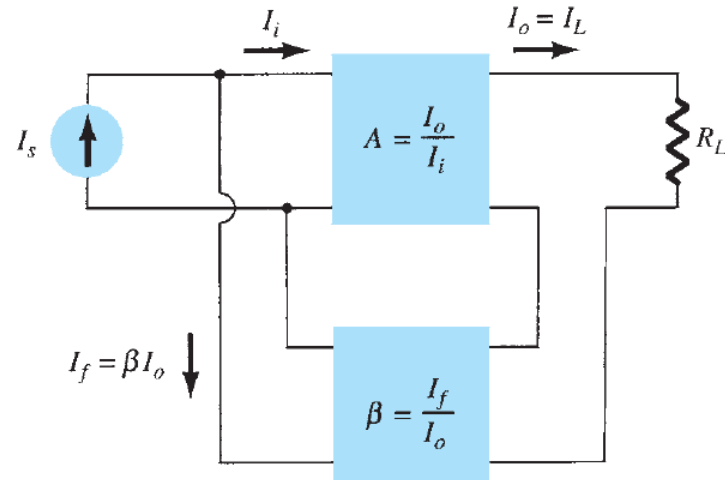


**Current-shunt feedback**

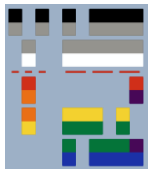

# Feedback Connection Types

## Summary of Gain, Feedback and Gain with Feedback

		Voltage-Series	Voltage-Shunt	Current-Series	Current-Shunt
Gain without feedback	$A$	$\frac{V_o}{V_i}$	$\frac{V_o}{I_i}$	$\frac{I_o}{V_i}$	$\frac{I_o}{I_i}$
Feedback	$\beta$	$\frac{V_f}{V_o}$	$\frac{I_f}{V_o}$	$\frac{V_f}{I_o}$	$\frac{I_f}{I_o}$
Gain with feedback	$A_f$	$\frac{V_o}{V_s}$	$\frac{V_o}{I_s}$	$\frac{I_o}{V_s}$	$\frac{I_o}{I_s}$

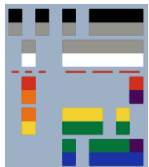



# Voltage-Series Feedback

When there is no feedback:

$$A = \frac{V_o}{V_s} = \frac{V_o}{V_i}$$



When  $V_f$  is connected in series with the input:

$$\begin{aligned} V_i &= V_s - V_f \\ V_o &= AV_i = A(V_s - V_f) = AV_s - AV_f \\ V_o &= AV_s - A\beta V_o \\ (1 + \beta A)V_o &= AV_s \\ A &\rightarrow A_f \end{aligned}$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A} = \text{overall gain of feedback amplifier (decreased by } 1 + \beta A)$$

$$A = \frac{V_o}{V_i} = \text{gain of amplifier when there is no feedback}$$
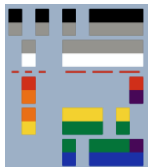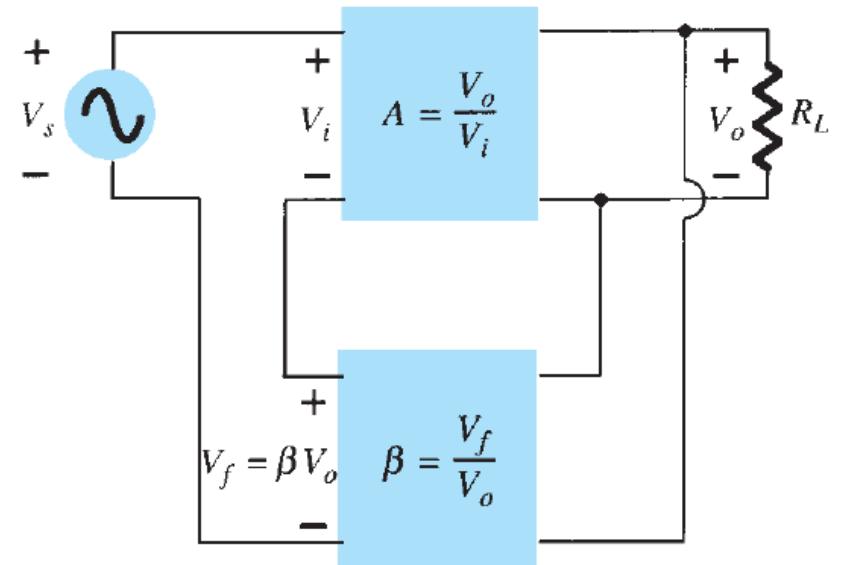
$$\beta = \frac{V_f}{V_o} = \text{feedback}$$



# Voltage-Shunt Feedback

When there is no feedback:

$$A = \frac{V_o}{I_i} = \frac{V_o}{I_s}$$



When a feedback signal is connected in parallel with the input is connected in parallel with the input:

$$A_f = \frac{V_o}{I_s} = \frac{AI_i}{I_i + I_f} = \frac{AI_i}{I_i + \beta V_o} = \frac{AI_i}{I_i + \beta AI_i}$$


$$A_f = \frac{A}{1 + \beta A} = \text{overall gain of feedback amplifier (decreased by } 1 + \beta A)$$

$$A = \frac{V_o}{I_i} = \text{gain of amplifier when there is no feedback}$$
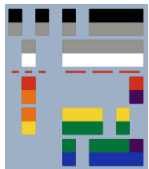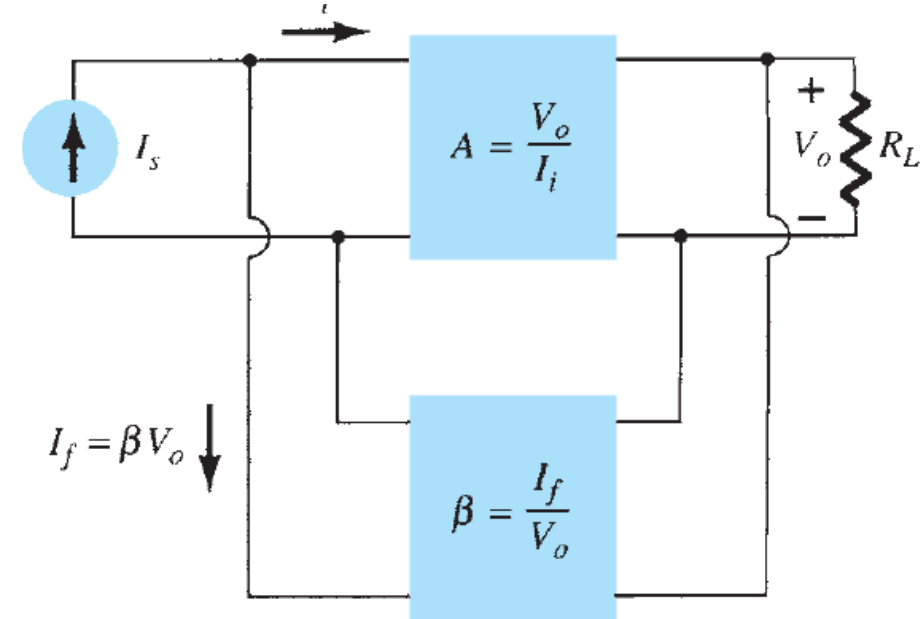
$$\beta = \frac{I_f}{V_o} = \text{feedback}$$



# Input Impedance (Voltage Series)

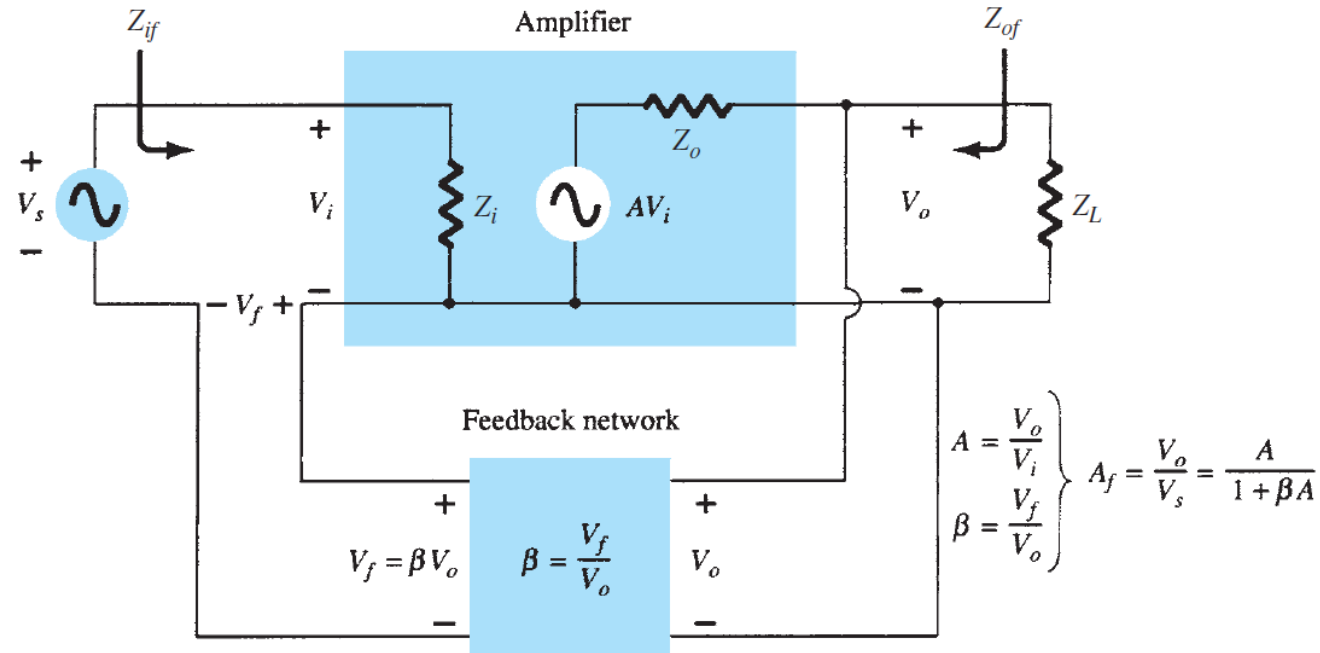


$$I_i = \frac{V_i}{Z_i} = \frac{V_s - V_f}{Z_i} = \frac{V_s - \beta V_o}{Z_i} = \frac{V_s - \beta A V_i}{Z_i}$$


$$I_i Z_i = V_s - \beta A V_i$$

$$V_s = I_i Z_i + \beta A V_i = I_i Z_i + \beta A I_i Z_i$$
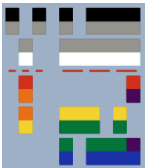
$$Z_{if} = \frac{V_s}{I_i} = Z_i + (\beta A) Z_i = Z_i (1 + \beta A)$$




# Input Impedance (Voltage Shunt)

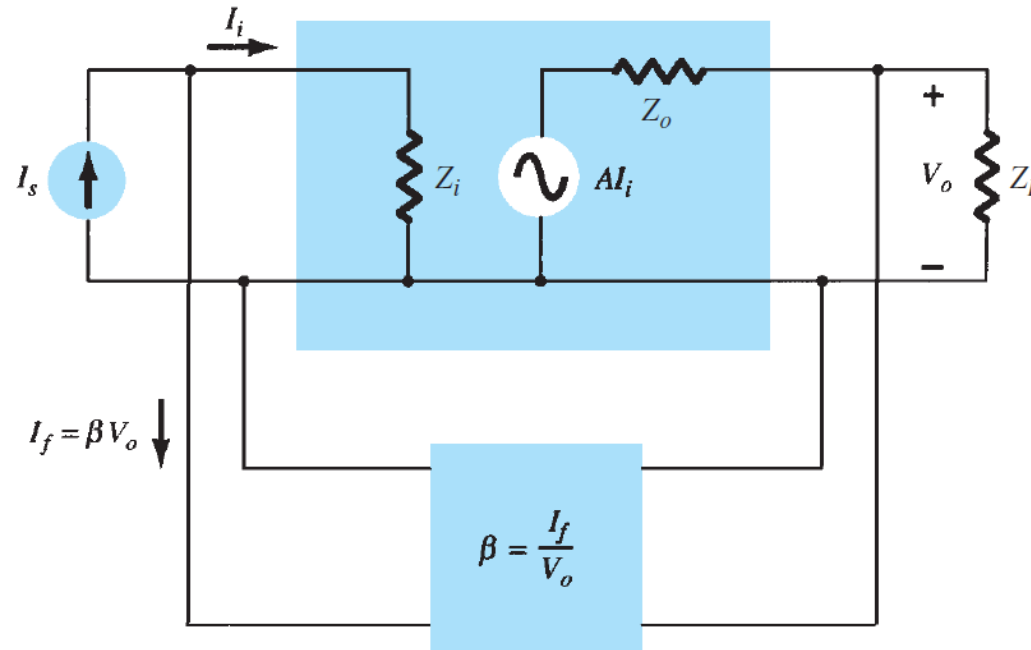

$$Z_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i + I_f} = \frac{V_i}{I_i + \beta V_o}$$

$$Z_{if} = \frac{V_i/I_i}{I_i/I_i + \beta V_o/I_i}$$

$$Z_{if} = \frac{Z_i}{1 + \beta A}$$

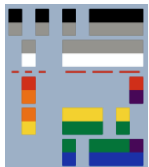

# Output Impedance

Voltage Series Feedback

$$Z_{of} = \frac{Z_o}{(1 + \beta A)}$$

Voltage Shunt Feedback

$$Z_{of} = \frac{Z_o}{(1 + \beta A)}$$

Current Series Feedback

$$Z_{of} = Z_o(1 + \beta A)$$


Current Shunt Feedback

$$Z_{of} = Z_o(1 + \beta A)$$




# Impedances Summary

Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
$Z_{if} = Z_i(1 + \beta A)$ (increased)	$Z_i(1 + \beta A)$ (increased)	$\frac{Z_i}{1 + \beta A}$ (decreased)	$\frac{Z_i}{1 + \beta A}$ (decreased)
$Z_{of} = \frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o(1 + \beta A)$ (increased)	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o(1 + \beta A)$ (increased)

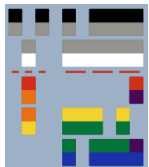

# Effects of Negative Feedback

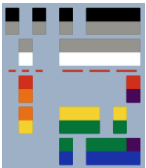

# Reduction in Frequency Distortion

- For a negative-feedback amplifier having  $\beta A \gg 1$ , the gain with feedback is  $A_f \cong 1/\beta$
- This value indicates that the feedback network is purely resistive and the gain of the feedback is not dependent on frequency (even the gain is dependent on the frequency).
- The frequency distortion arising because of varying amplifier gain with frequency is considerably reduced in a negative-voltage feedback amplifier circuit.





# Reduction in Noise and Nonlinear Distortion

- Signal feedback tends to hold down the amount of noise signal (such as power-supply hum) and nonlinear distortion.
- The factor  $(1+\beta A)$  reduces the input noise and improvement of nonlinear distortion. As trade-off, there is a reduction in overall gain.
- An additional amplifier stage will increase the overall gain but it will introduce as much noise (reduced by the feedback amplifier).
- This may be improved by readjusting the gain of the feedback amplifier circuit to obtain higher gain while also providing reduced noise signal.



# Gain and Bandwidth



- The overall gain with negative feedback is described by the equation:

$$A_f = \frac{A}{1+\beta A} \cong \frac{A}{\beta A} = \frac{1}{\beta} \text{ for } \beta A \gg 1$$



- As long  $\beta A \gg 1$ , the overall gain is approximately  $1/\beta$ .
- In a basic amplifier, the open loop gain has open-loop drops because of the active devices and capacitances at high frequencies.
- At low frequencies for capacitively coupled amplifier stages the gain may also drop.
- Once the open-loop gain  $A$  drops low enough and the factor  $\beta A \gg 1$ , then based on the equation described by  $A_f \cong 1/\beta$  is no longer holds true.



# Gain and Bandwidth

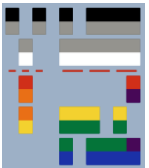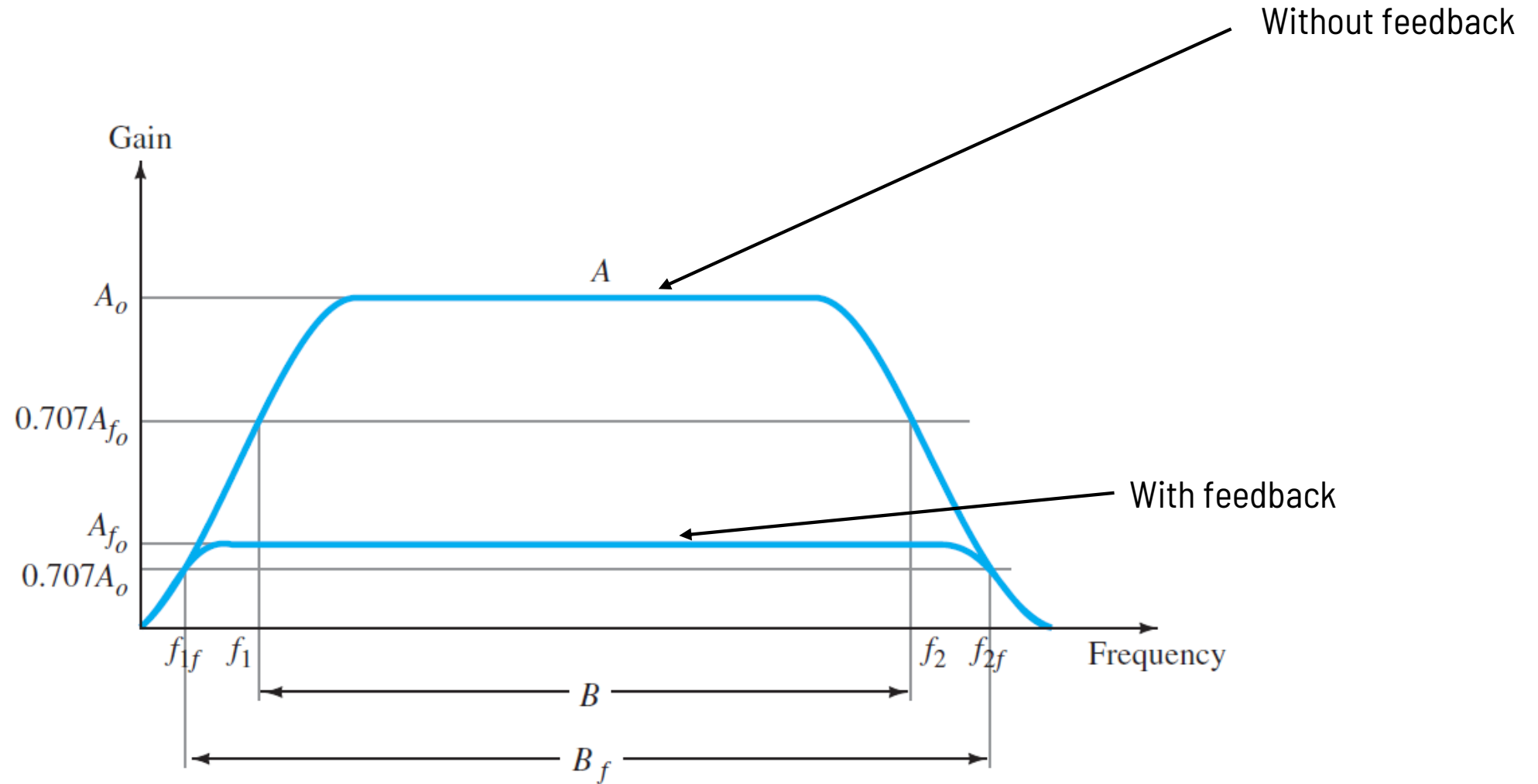

# Gain and Bandwidth

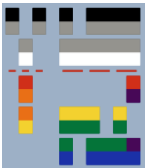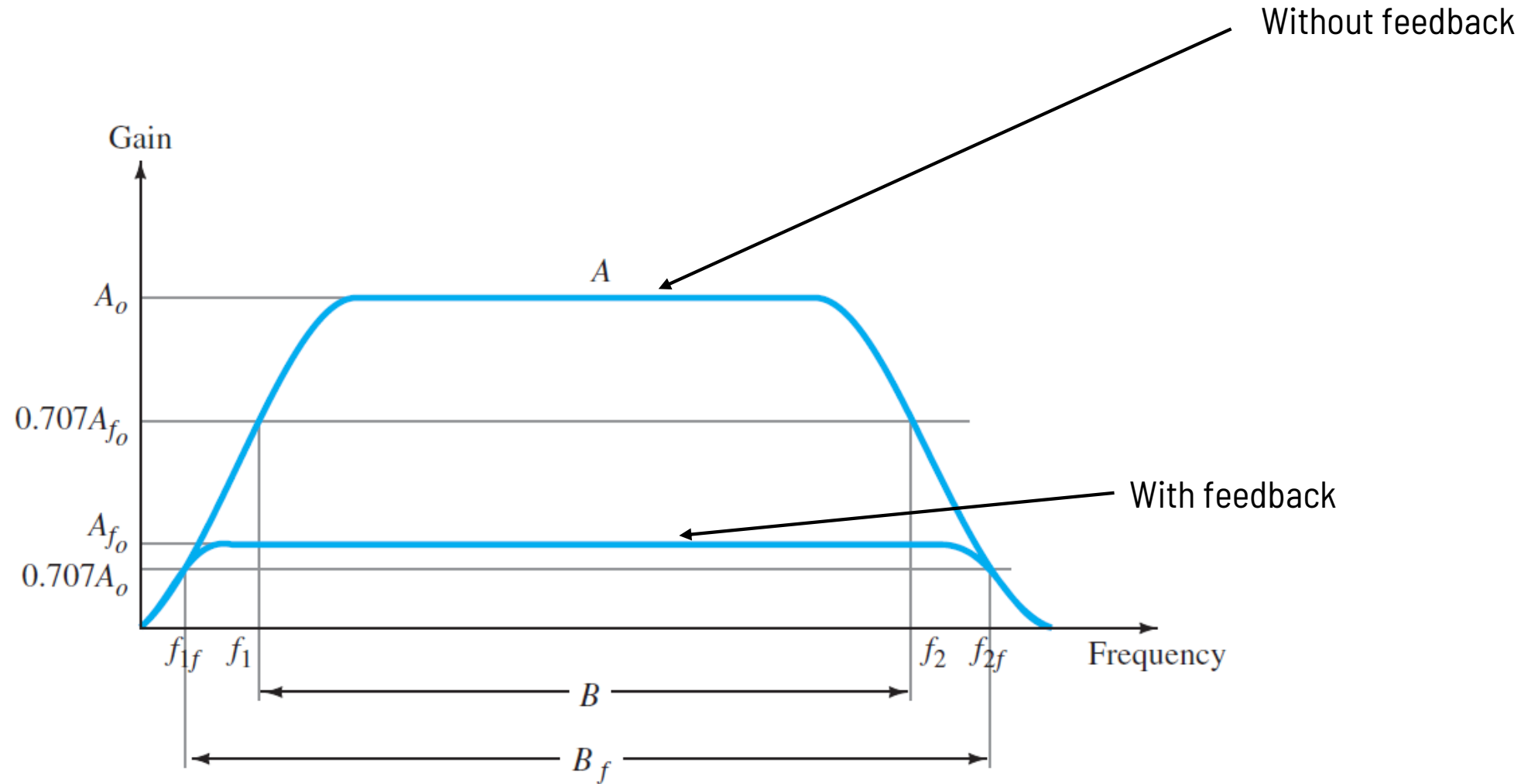


# Gain Stability


- Differentiating the gain equation with feedback:

$$\left| \frac{dA_F}{A_f} \right| = \frac{1}{|1 + \beta A|} \left| \frac{dA}{A} \right|$$
$$\left| \frac{dA_f}{A_f} \right| \cong \left| \frac{1}{\beta A} \right| \left| \frac{dA}{A} \right| \text{ for } \beta A \gg 1$$



- The magnitude of the relative change in gain ( $\left| \frac{dA_F}{A_f} \right|$ ) is reduced by the factor  $|\beta A|$  compared to that with feedback ( $\left| \frac{dA}{A} \right|$ )

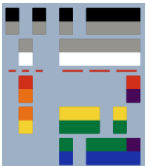

# Feedback Amplifier Circuits

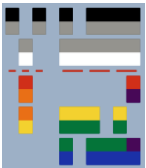

# Voltage Series Feedback

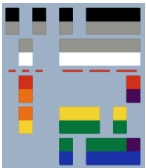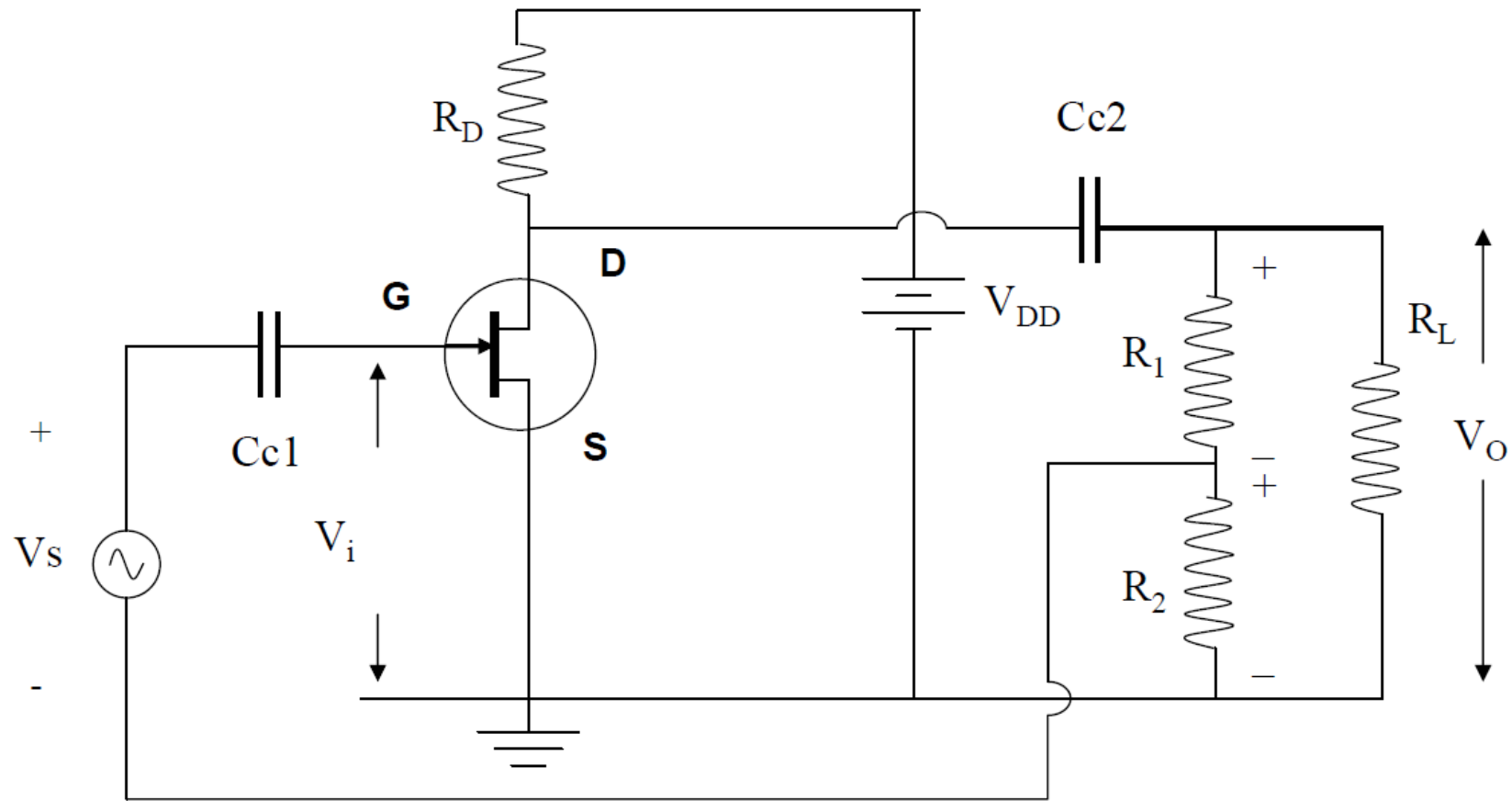

# Voltage Series Feedback

$$A = \frac{V_o}{V_s} = \frac{V_o}{V_i} =$$



$$A = -g_m(r_d \parallel R_D \parallel R_L \parallel (R_1 + R_2))$$

$$\beta = \frac{V_f}{V_o} = -\frac{R_2}{R_1 + R_2}$$

The overall gain of the feedback FET Amplifier is:

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$
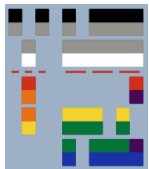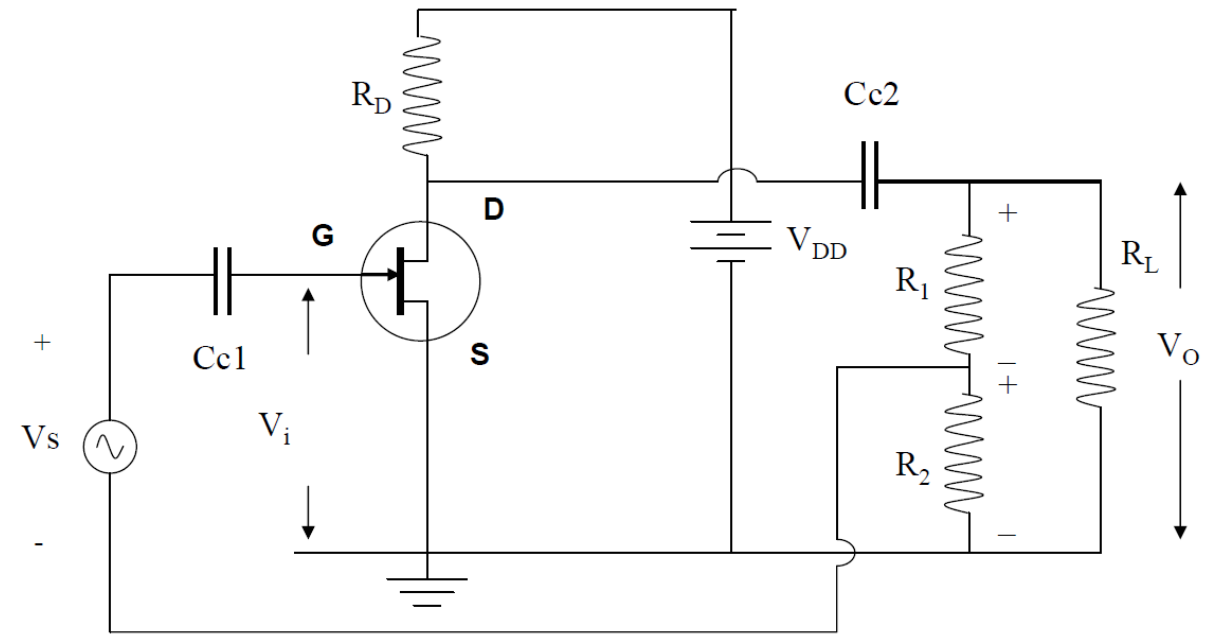
$$A_f = \frac{-g_m(r_d \parallel R_D \parallel R_L \parallel (R_1 + R_2))}{1 + \left[ \frac{R_2}{R_1 + R_2} \right] g_m(r_d \parallel R_D \parallel R_L \parallel (R_1 + R_2))}$$





# Voltage Shunt Feedback

$$A = \frac{V_o}{I_i} = \infty$$



$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_o}$$

The transfer resistance gain with feedback

$$A_f = \frac{V_o}{V_s} = \frac{V_o}{I_i} = \frac{A}{1 + \beta A} = \frac{1}{\beta} = -R_o$$

The usual gain
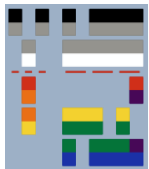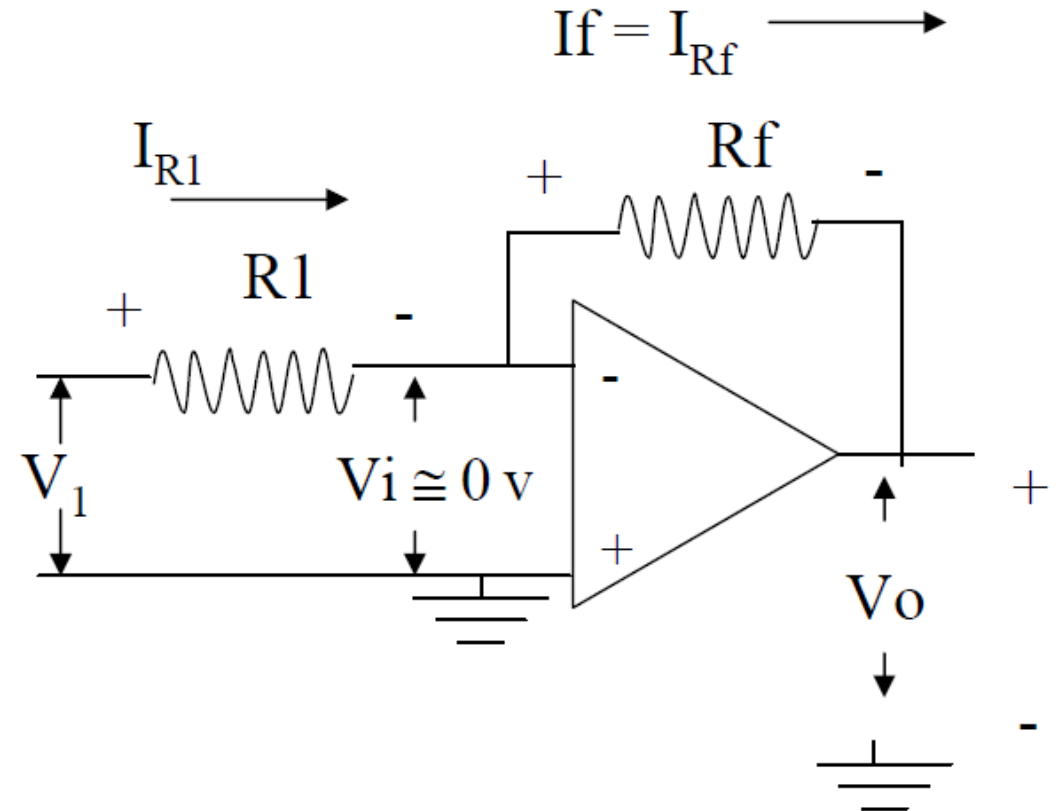
$$A_f = \frac{V_o}{I_s} \frac{I_s}{V_1} = (-R_o) \frac{1}{R_1} = \frac{-R_o}{R_1}$$



# Current Series Feedback


$$I_{R1} = I_s = \frac{V_1}{R_1}$$

$$A = \frac{V_o}{I_i} = \infty$$

$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_f}$$

$$A_f = \frac{V_o}{I_s} = \frac{V_o}{I_i} = \frac{A}{1 + \beta A} = -R_f$$
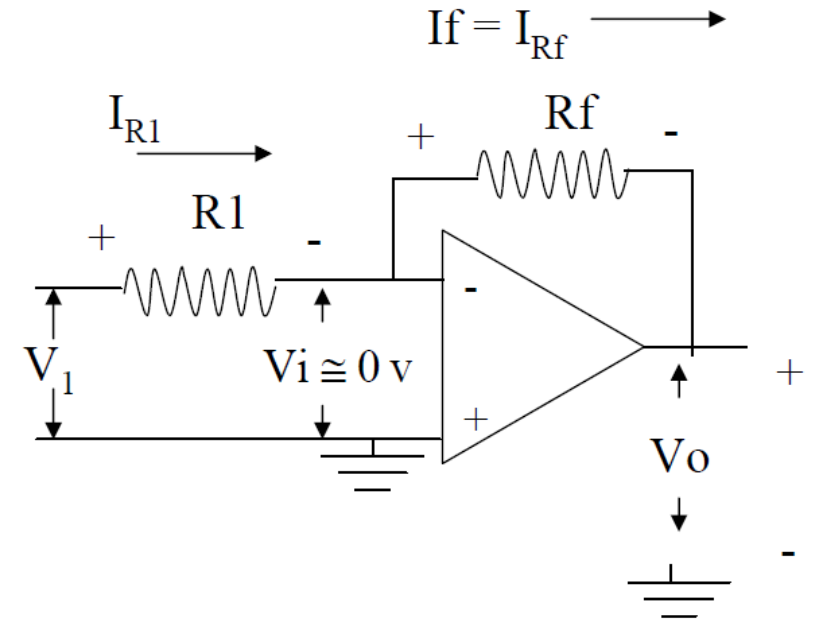
$$A_{vf} = \frac{V_o}{V_1} = \frac{V_o}{I_s} \frac{I_s}{V_1} = -\frac{R_f}{R_1}$$



End

