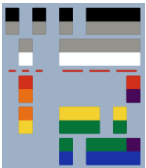




# PASSIVE FILTERS




# Topic Outcomes

- Describe different types and components of passive filters.
- Analyze the frequency response of passive filters
- Discuss methods of measuring frequency response, critical frequency, and bandwidth thru computations.




# Filters

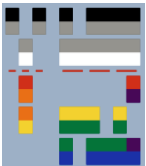

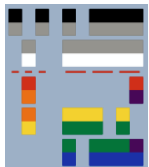
# Filters

- In telecommunications and signal processing, it is very useful to separate a specific bandwidth from the total spectrum.
- A filter is a circuit that allows certain range of frequencies to pass and attenuates all the other frequencies.
- The range of frequencies allowed to pass through filter is called the passband.
- The passband should have a minimum attenuation of  $<-3\text{dB}$ .
- The end of the passband is called the critical frequency or cutoff frequency ( $f_c$ )
- The critical frequency is the point where the response drops  $-3\text{dB}$  from the passband.
- The transition region and the stopband regions are the regions after the passband.



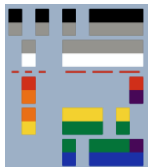
# Filters

- Filters can be categorized into two types: passive and active.
- The four general categories of filter according to their response are:
  - Low-pass filter- allow frequencies below the cutoff frequency and reject all frequencies above the cutoff frequency.
  - High-pass filter – allow frequencies above the cutoff frequency and reject all frequencies below the cutoff frequency.
  - Band-pass filter – allows frequencies within a band or range of frequencies and reject all frequencies outside the band
  - Band-stop/Band-reject filter – rejects frequencies within a band or range of frequencies and allows all other outside the band




# Filters


- Low-pass filter

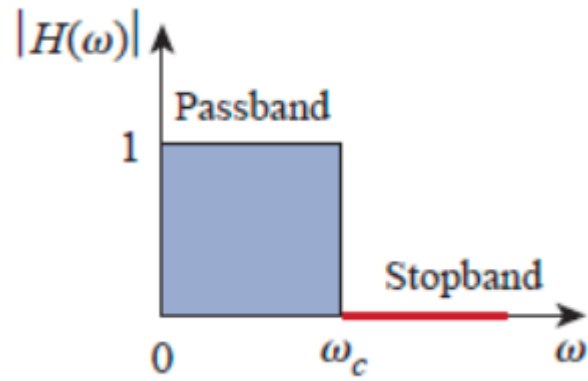



- High-pass filter

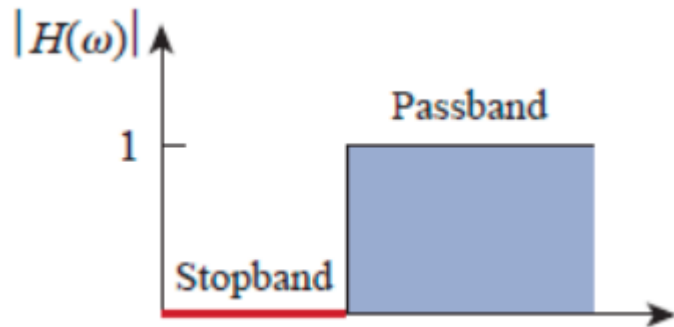


- Band-pass filter

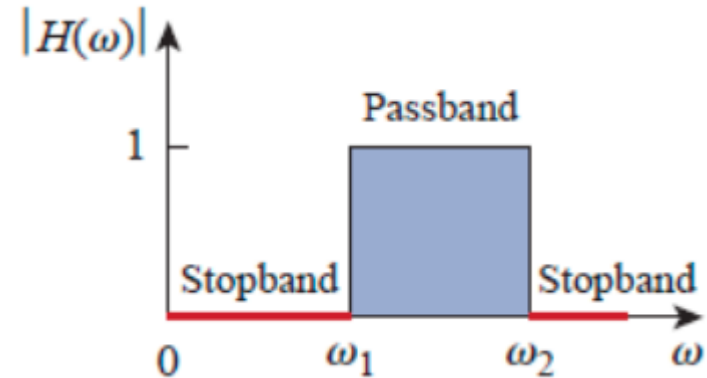

- Band-stop/Band-reject filter

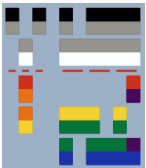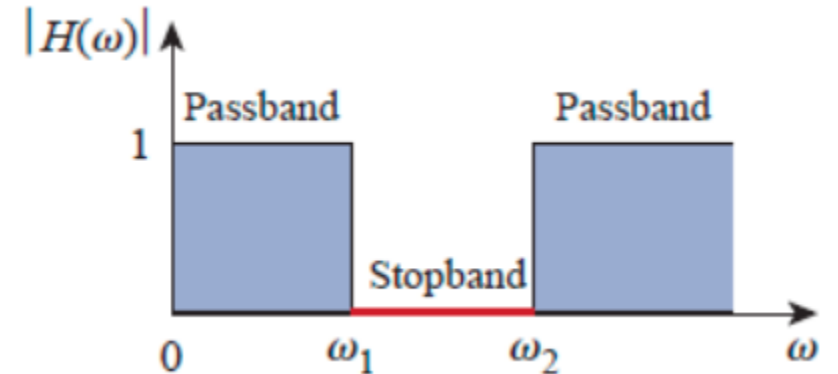

# Passive filters

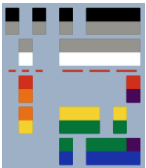

# Passive filters



- Use a combination of passive components: RC, RL and RLC circuit that only passes and rejects specific range of frequencies.
- No “active” (e.g. transistor, op-amps) components




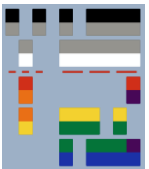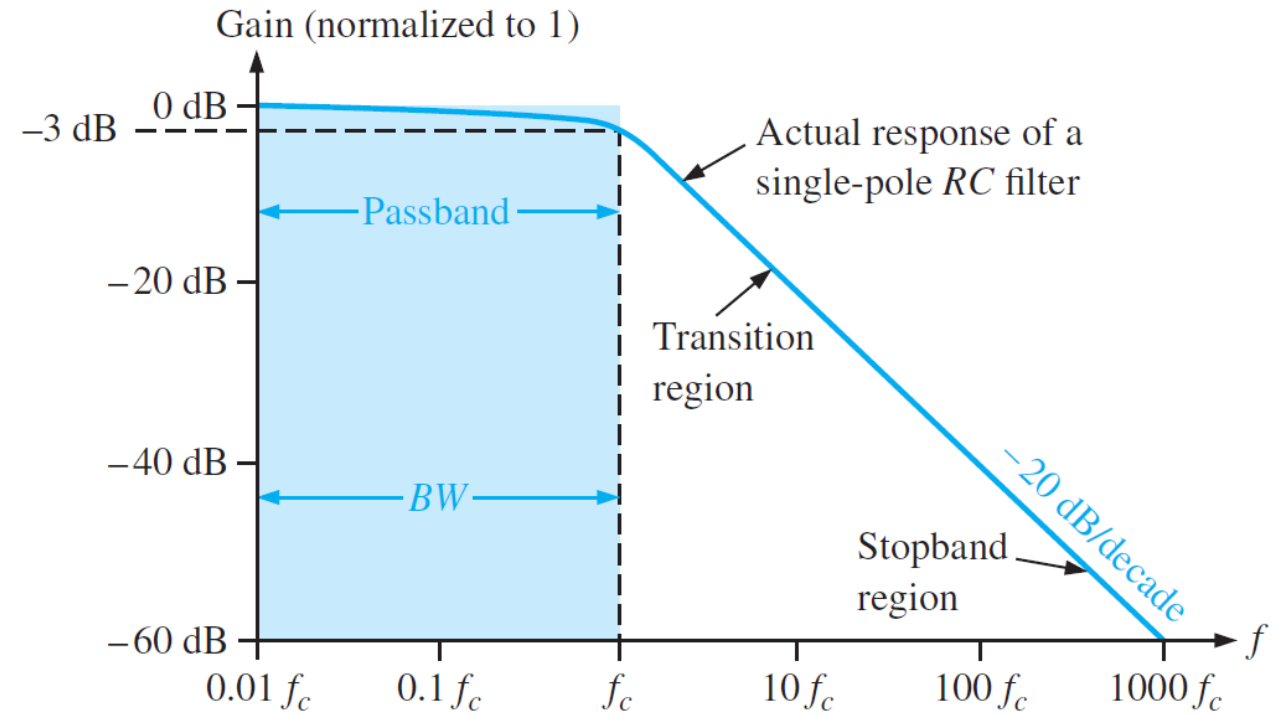
# Passive Low-Pass filters

- A low-pass filter is a circuit that passes the frequency range from DC (0 Hz) to  $f_c$  and attenuates all the other frequencies.
- The shaded region in the figure shows the ideal response ("brick-wall") of the low-pass filter.
- In this case **BW =  $f_c$**




# Passive Low-Pass filters

- The most basic low-pass filter is a simple RC circuit shown.
- The output is taken across the capacitor
- The circuit has a single pole and rolls off at - 20dB/decade beyond  $f_c$

$$f_c = \frac{1}{2\pi RC}$$

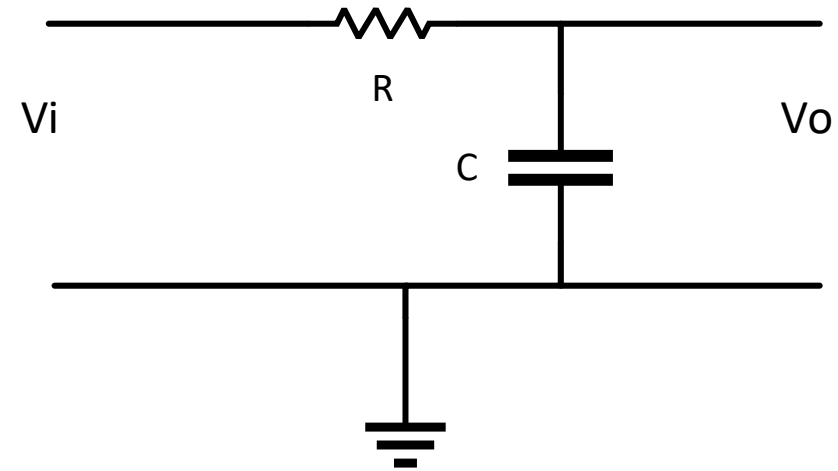- The output at the critical frequency is 70.7% of the input which is equivalent to an attenuation of -3dB



- The most basic low-pass filter is a simple RC circuit shown.
- The output is taken across the capacitor
- The circuit has a single pole and rolls off at - 20dB/decade beyond  $f_c$



$$f_c = \frac{1}{2\pi RC}$$

- The output at the critical frequency is 70.7% of the input which is equivalent to an attenuation of -3dB



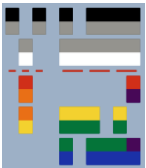
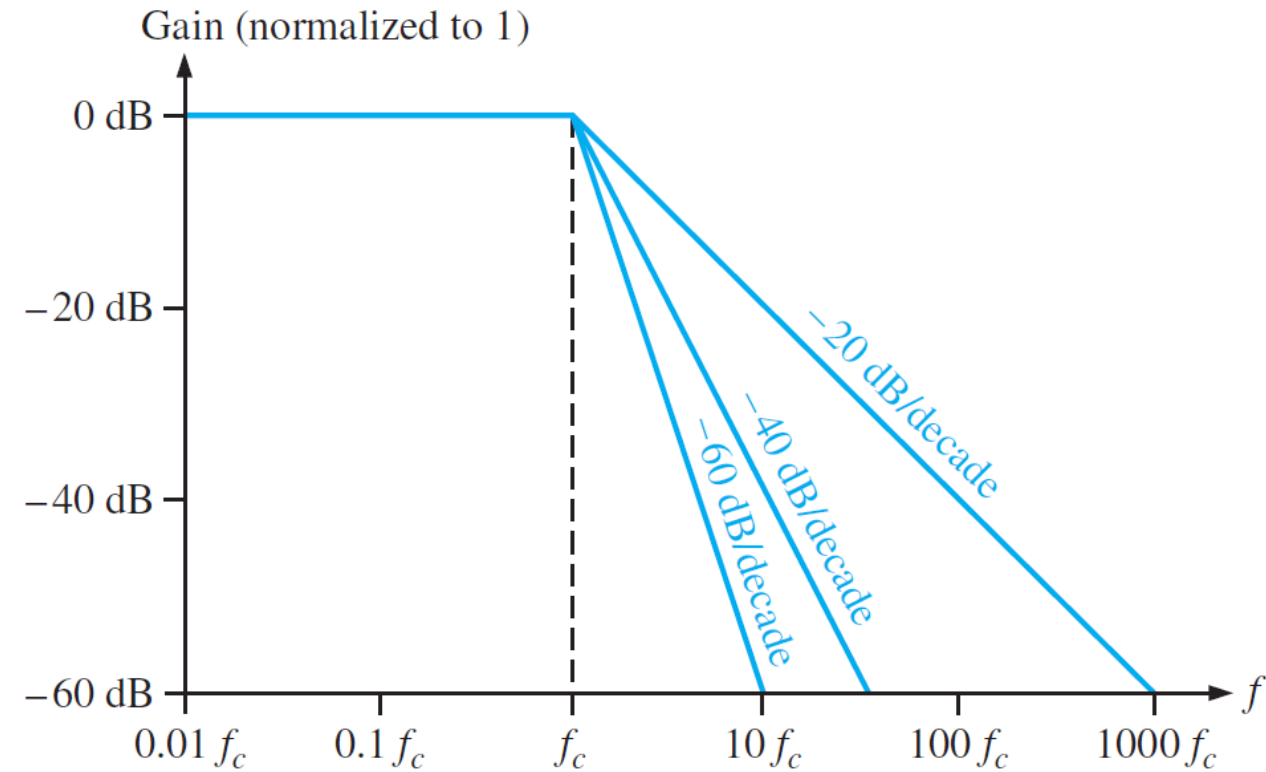
# Passive Low-Pass filters

- The figure shows the idealized response of the basic low-pass filter circuit.
- It shows a flat response up to the cut-off frequency and a constant roll-off rate after the cutoff frequency which the actual filter doesn't have.
- The addition of circuit components in a basic filter will produce a steeper region which is more effective.





# Passive Low-Pass filters

$$f_c = \frac{R}{2\pi L}$$

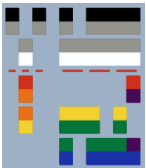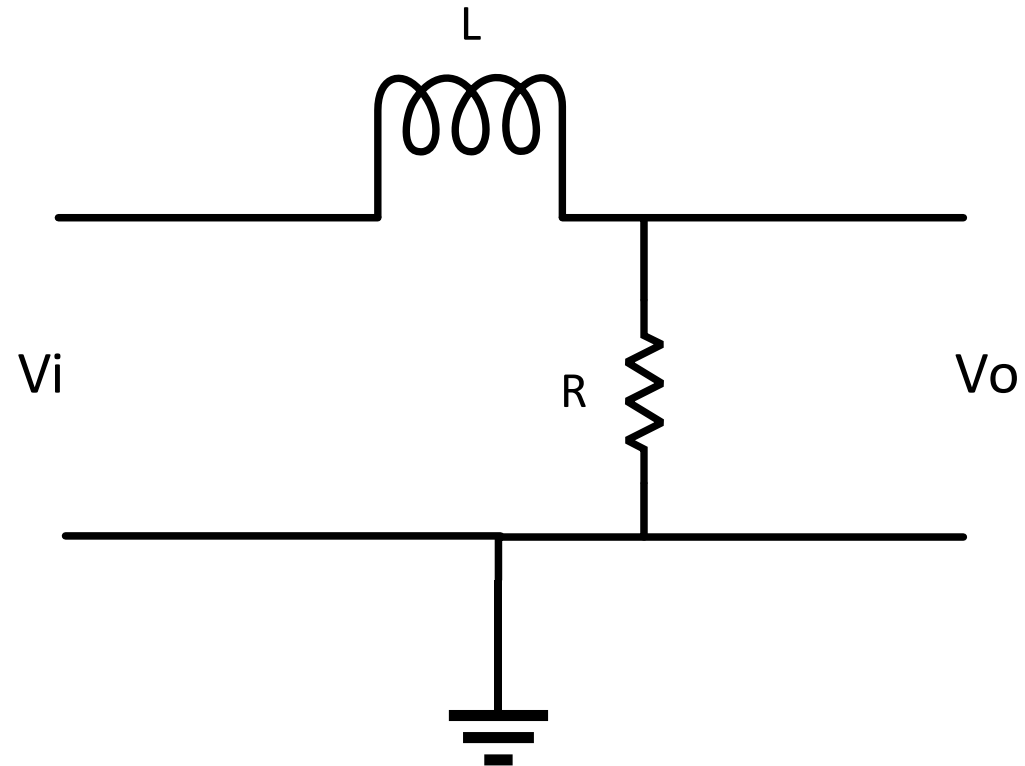
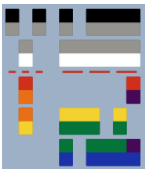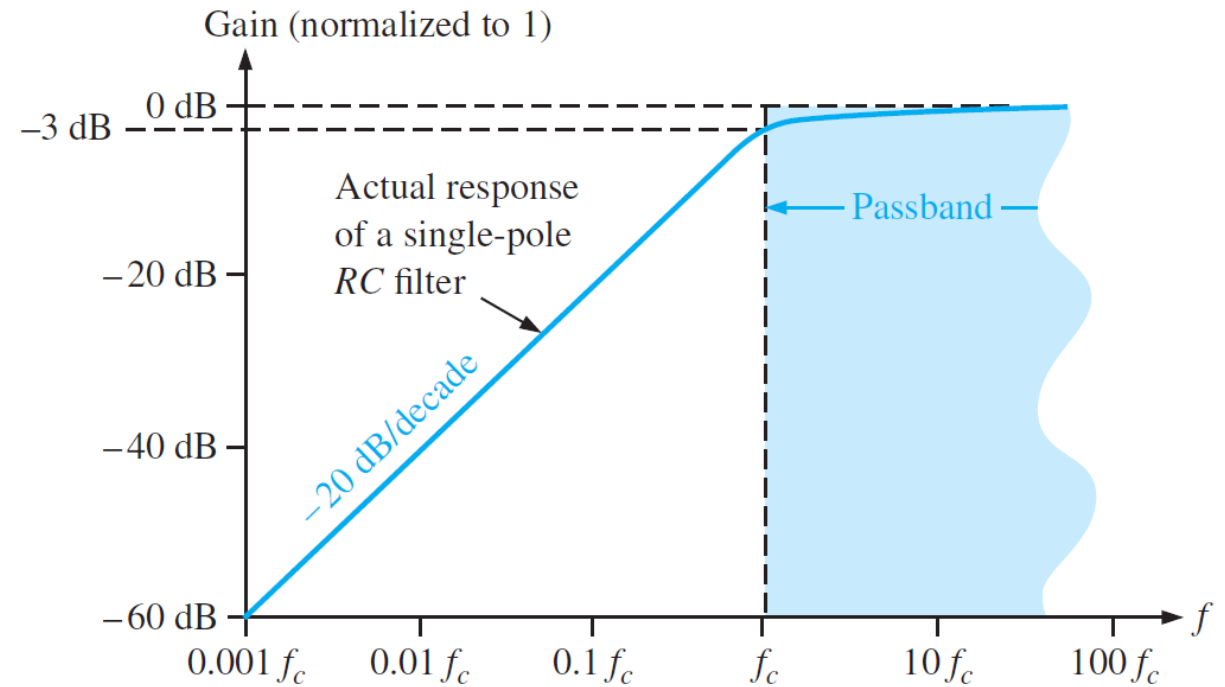
# Passive High-Pass filters



- A high-pass filter rejects all frequencies below critical frequency and passes all frequencies above  $f_c$
- At the critical frequency the output is 70.7% of the input (-3 dB attenuation).
- Ideally the passband of a high-pass filter is all frequencies above the critical frequency



# Passive High-Pass filters

$$f_c = \frac{1}{2\pi RC}$$

$$f_c = \frac{R}{2\pi L}$$

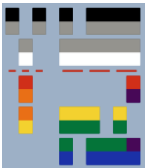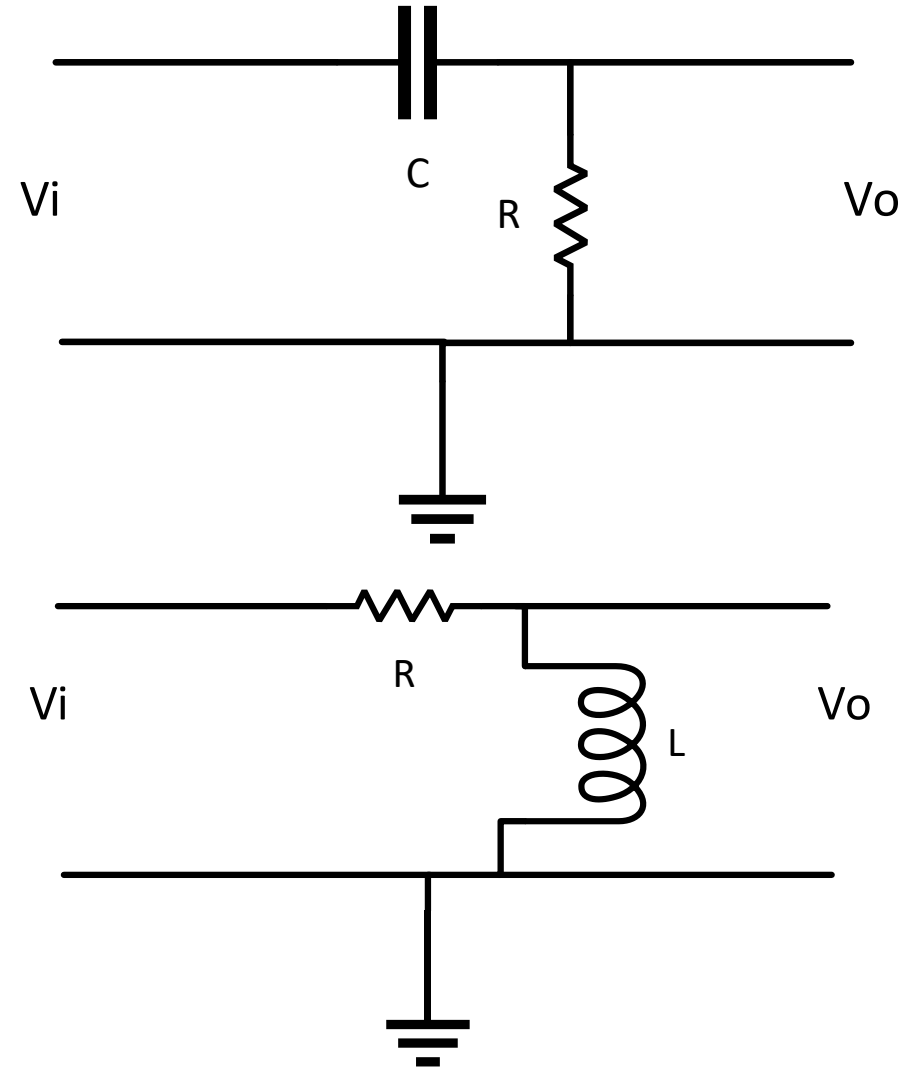


# Passive Band-Pass filters

- A band-pass filter allows a certain range to pass and rejects all frequencies above and below the passband.
- The typical band-pass filter is shown in the figure.


$$BW = f_{c_2} - f_{c_1}$$

- The center frequency  $f_0$  is:


$$f_0 = \sqrt{f_{c_1} f_{c_2}}$$

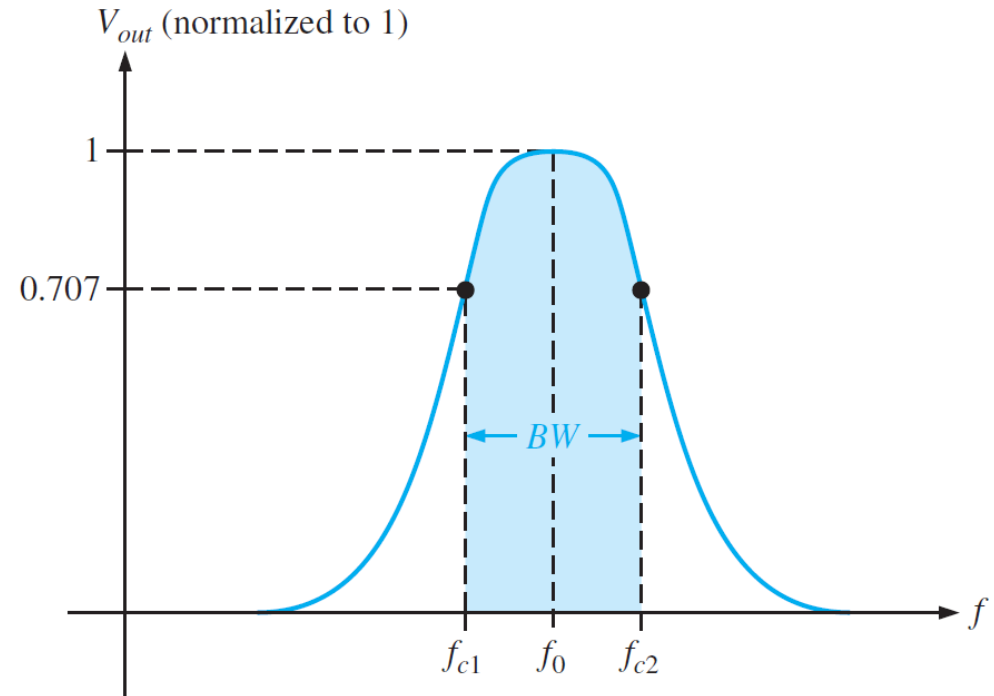

# Passive Band-Pass filters

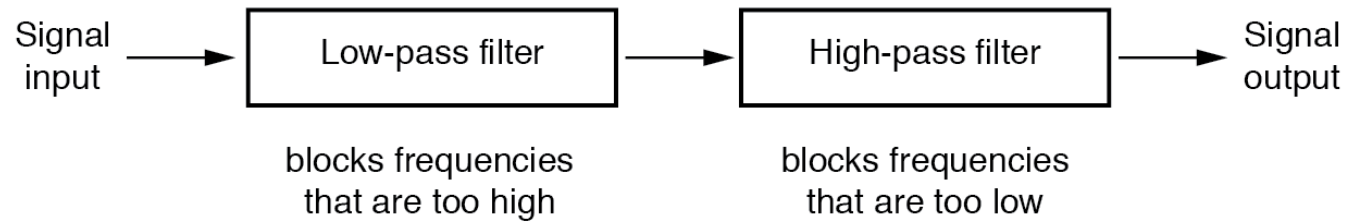

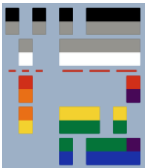- A simple band-pass filter can be constructed by cascading a low-pass filter with a high-pass filter.
- If  $f_{C_1}$  (high-pass filter cutoff) is higher than  $f_{C_2}$  (low-pass filter cutoff), the responses may overlap and all the frequency beyond the two critical frequencies are eliminated.







# Quality factor, $Q$

- The quality factor ( $Q$ ) of a band-pass filter is the ratio of the center frequency to the bandwidth.


$$Q = \frac{f_o}{BW}$$

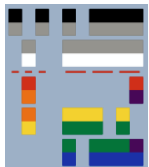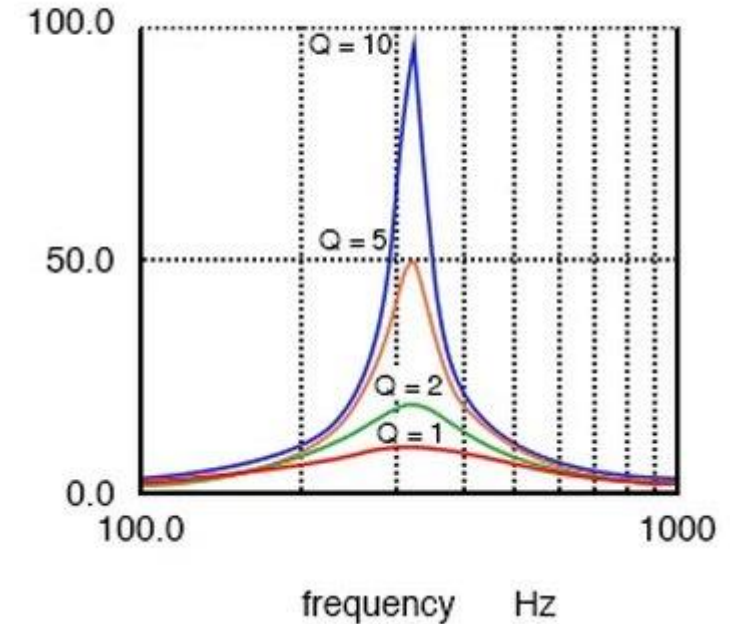- Higher  $Q$  means narrower bandwidth for the filter.
- This also results to better selectivity for a certain value of center frequency.
- Band-pass filters are also classified as narrow-band ( $Q > 10$ ) or wide-band ( $Q < 10$ )



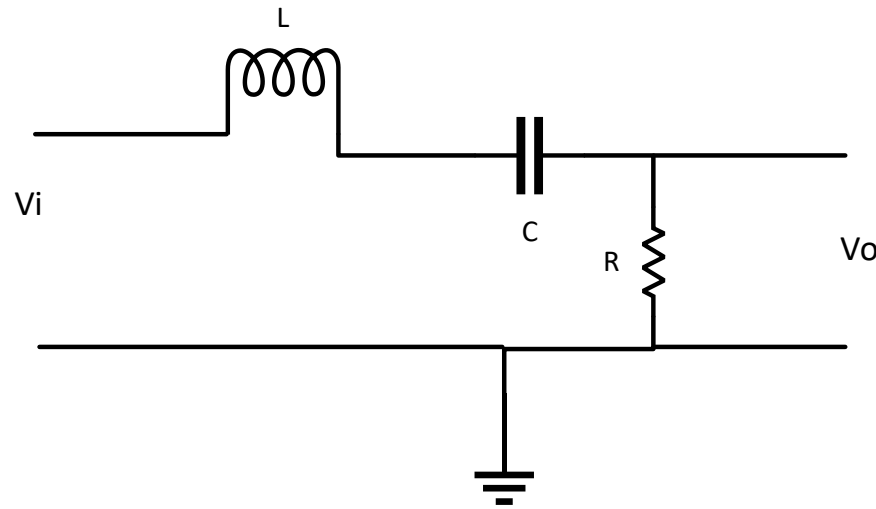
# Passive Band-Pass Filter

- Series Resonant Band-Pass Filter Circuit



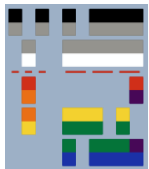
$$Q = \frac{X_L}{R}, BW = \frac{f_o}{Q}, f_o = \frac{1}{2\pi\sqrt{LC}}$$



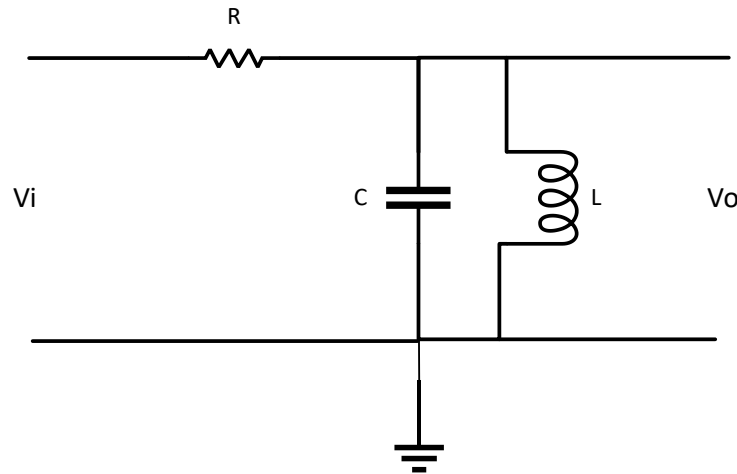
# Passive Band-Pass Filter

- Parallel Resonant Band-Pass Filter Circuit




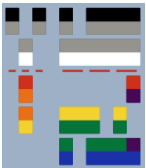
$$Q = \frac{X_L}{R}, BW = \frac{f_o}{Q}, f_o = \frac{1}{2\pi\sqrt{LC}}$$



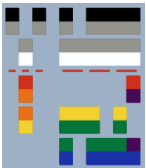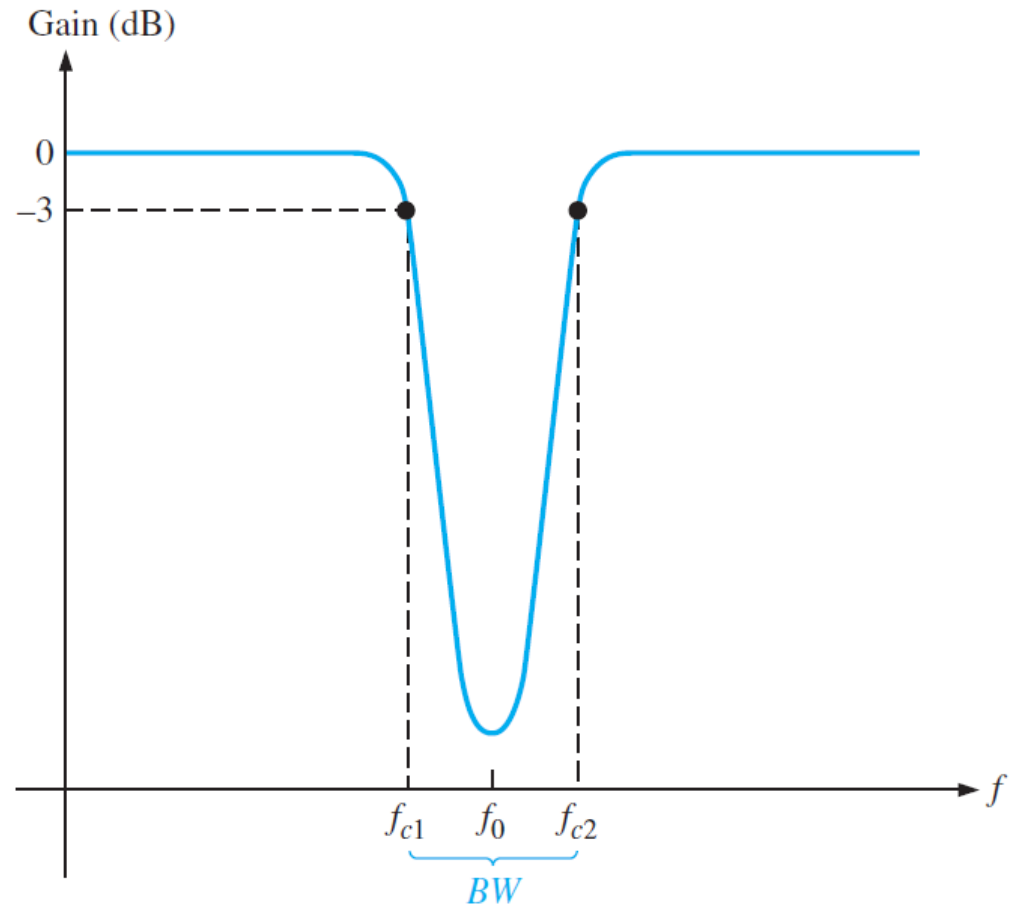
# Passive Band-Stop Filter

- A band-stop filter is an opposite of a band-pass filter when it comes to responses.
- This type of filter allows all the frequencies to pass except those lying in a certain range of frequencies.



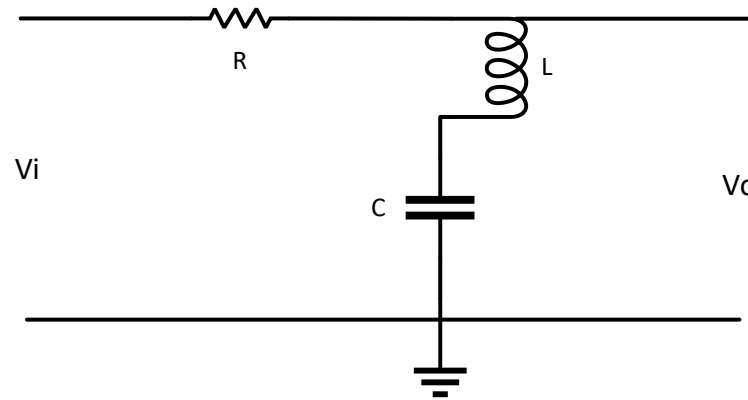
# Passive Band-Stop Filter

- Series Resonant Band-Stop Filter Circuit



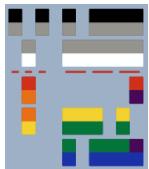
$$Q = \frac{X_L}{R}, BW = \frac{f_o}{Q}, f_o = \frac{1}{2\pi\sqrt{LC}}$$



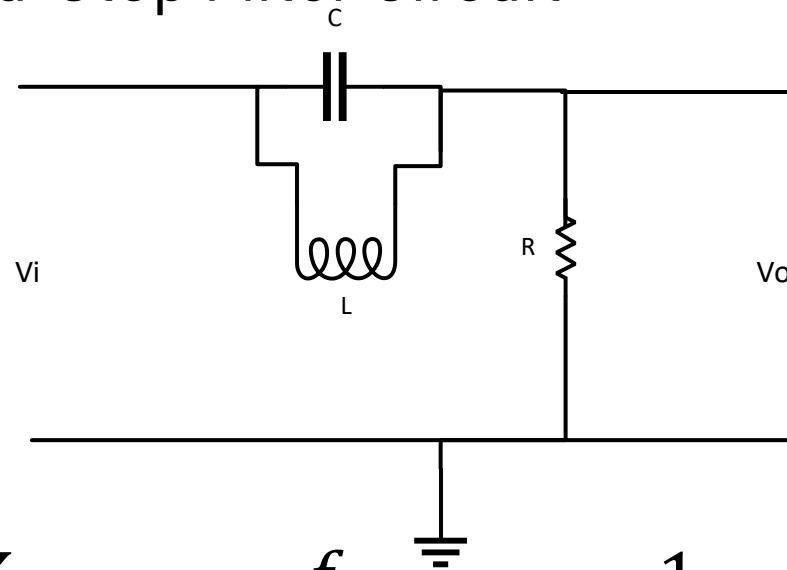
# Passive Band-Stop Filter

- Parallel Resonant Band-Stop Filter Circuit


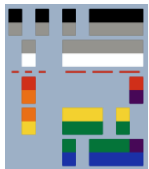
$$Q = \frac{X_L}{R}, BW = \frac{f_o}{Q}, f_o = \frac{1}{2\pi\sqrt{LC}}$$



End

